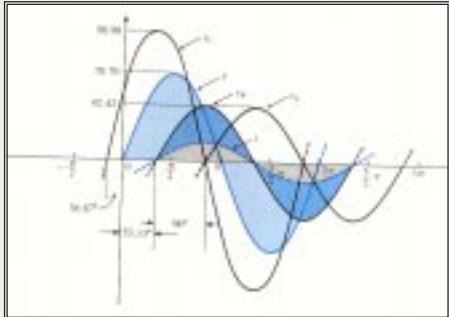



# CIRCUIT ANALYSIS II

## Chapter 1
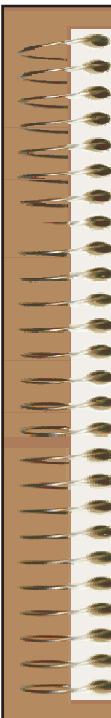
### Sinusoidal Alternating Waveforms and Phasor Concept



Dr. Adel Gastli      Sinusoidal Alternating Waveforms and Phasor Concept      1



## CONTENTS


- 1.1 Sinusoidal Alternating Waveforms
  - 1.1.1 General Format for the Sinusoidal Voltage & Current
  - 1.1.2 Average Value
  - 1.1.3 Effective Values
- 1.2 Basic Elements and Phasors
  - 1.2.1 Elements
  - 1.2.2 Average Power and Power Factor
  - 1.2.3 Rectangular and Polar Representation
  - 1.2.4 Impedance and Phasor Diagram
  - 1.2.5 Kirchhoff's Laws
- 1.3 Series and Parallel Circuits
  - 1.3.1 Series Circuits
  - 1.3.2 Parallel Circuits

Dr. Adel Gastli      Sinusoidal Alternating Waveforms and Phasor Concept      2

# 1.1 Sinusoidal Alternating Waveforms
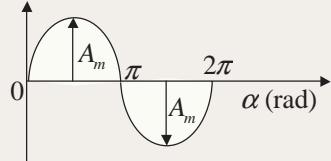
## 1.1.1 General Format for the Sinusoidal Voltage & Current


$A_m \sin \alpha = A_m \sin \omega t$  Basic mathematical format for the sinusoidal waveform




$$i = I_m \sin \omega t = I_m \sin \alpha$$

$$e = E_m \sin \omega t = E_m \sin \alpha$$

### Phasor Relations

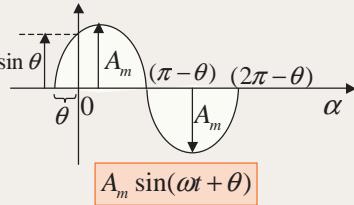

$$A_m \sin(\omega t + \theta)$$

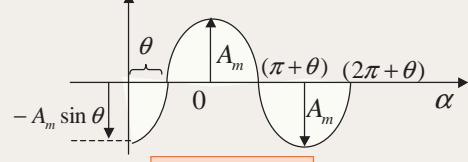

$$A_m \sin(\omega t - \theta)$$


Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

3
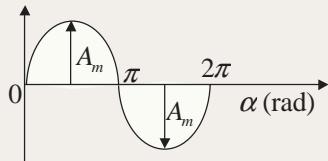
## 1.1.2 Average Value:

$$G \text{ (average value)} = \frac{\text{algebraic sum of the areas}}{\text{length of the curve}}$$



$$G = \frac{\int_0^{2\pi} A_m \sin \alpha}{2\pi} = 0$$

The average value of  
a pure sinusoidal  
waveform over one  
full cycle is zero.


If the waveform equation is:  $a = A_0 + A_m \sin \alpha$   
then the average value is:  $G = A_0$

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

4

### 1.1.3 Effective Values:

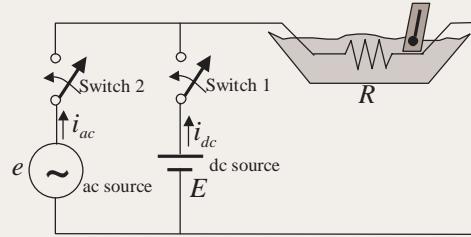

**The effective value of an ac current is the equivalent dc current that delivers the same power as the ac current.**

$$P_{ac} = i_{ac}^2 R = (I_m \sin \omega t)^2 R = (I_m^2 \sin^2 \omega t) R \quad \sin^2 \omega t = \frac{1}{2}(1 - \cos 2\omega t)$$

$$P_{ac} = \frac{I_m^2 R}{2} - \frac{I_m^2 R}{2} \cos 2\omega t$$

The average power delivered is:  $P_{av(ac)} = \frac{I_m^2 R}{2}$

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

5

Equating the average power delivered by the ac generator to that delivered by the dc source,

$$P_{av(ac)} = P_{dc} \sum \frac{I_m^2 R}{2} = I_{dc}^2 R \sum I_m = \sqrt{2} I_{dc}$$

$$I_{dc} = \frac{1}{\sqrt{2}} I_m = 0.707 \times I_m \quad \Rightarrow \quad I_{eff} = \frac{1}{\sqrt{2}} I_m = 0.707 \times I_m$$

Same thing for the voltage:

$$E_{eff} = \frac{1}{\sqrt{2}} E_m = 0.707 \times E_m$$

In general, the effective value of any quantity plotted as a function of time can be found by using the following equation:

$$I_{eff} = \sqrt{\frac{\int_0^T i^2 dt}{T}} = \sqrt{\frac{\text{area}(i^2)}{T}}$$

This procedure gives us another designation for the effective value, the **root-mean-square (rms) value**.

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept



6

# 1.2 Basic Elements and Phasors
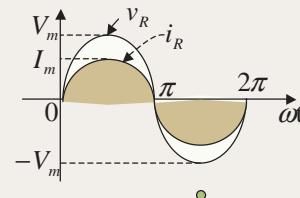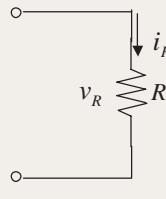
## 1.2.1 Elements

Response of the basic R, L and C elements to a sinusoidal voltage and current.

**Resistor:**  $i = \frac{v}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t \rightarrow I_m = \frac{V_m}{R} \Leftrightarrow V_m = I_m R$



*For a purely resistive element, the voltage across and the current through the element are in phase*

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept



7

### Inductor:

$$v_L = L \frac{di_L}{dt} = L \frac{d}{dt} (I_m \sin \omega t) = \omega L I_m \cos(\omega t) = V_m \sin(\omega t + 90^\circ)$$

$$\rightarrow V_m = \omega L I_m \quad X_L = \omega L : \text{reactance of the inductor (Ohms).}$$

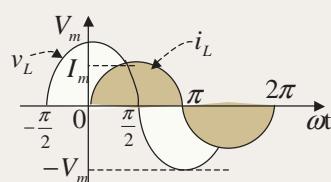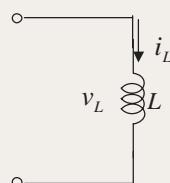Inductive reactance is the opposition to the flow of current, which results in the continual interchange of energy between the source and the magnetic field of the inductor. Unlike resistance, reactance does not dissipate electric energy.



*For an inductor  $v_L$  leads  $i_L$  by  $90^\circ$ , or  $i_L$  lags  $v_L$  by  $90^\circ$ .*

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept



8

### Capacitor:

$$i_c = C \frac{dv_c}{dt} = C \frac{d}{dt} (V_m \sin \omega t) = \omega C V_m \cos(\omega t) = I_m \sin(\omega t + 90^\circ)$$

$$\Rightarrow I_m = \omega C V_m \Leftrightarrow V_m = \frac{1}{\omega C} I_m \quad X_C = \frac{1}{\omega C} : \text{reactance of the capacitor (Ohms).}$$

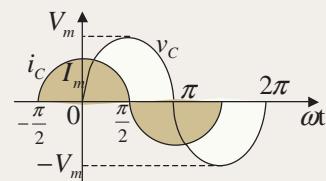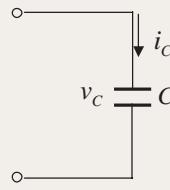Capacitive reactance is the opposition to the flow of charge, which results in the continual interchange of energy between the source and the electric field of the capacitor. Like the inductor, the capacitor does not dissipate electric energy.




For a capacitor  $i_c$  leads  $v_c$  by  $90^\circ$ , or  $v_c$  lags  $i_c$  by  $90^\circ$ .

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

9

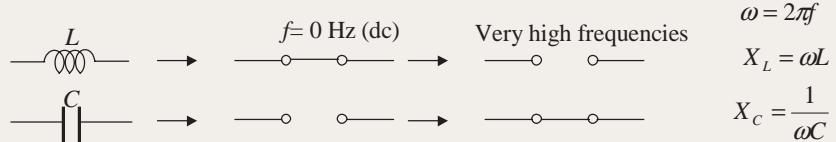As a general rule for circuit with combined elements: if the current leads the voltage, the circuit is predominantly capacitive, and if the voltage leads the current, it is predominantly inductive.



Instead of differentiation, it is possible to use integration depending on the unknown quantities:

$$i_L = \frac{1}{L} \int v_L dt$$

$$v_C = \frac{1}{C} \int i_C dt$$

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

10

## 1.2.2 Average Power and Power Factor

In general the instantaneous power is determined by:  $p = vi$

In general, for a sinusoidal voltage and current, the average power is determined by:

$$P = \frac{V_m I_m}{2} \cos \theta = V_{eff} I_{eff} \cos \theta$$

Where  $\theta$  is the phase angle between the voltage and the current.

$$V_{eff} = V_{rms} = \frac{V_m}{\sqrt{2}} \quad \text{Effective voltage}$$

$$I_{eff} = I_{rms} = \frac{I_m}{\sqrt{2}} \quad \text{Effective current}$$

$$PF = \cos \theta \quad \text{Power Factor}$$

**Resistor**

$$P = \frac{V_m I_m}{2} \cos 0 = V_{eff} I_{eff}$$

**Inductor**

$$P = \frac{V_m I_m}{2} \cos 90^\circ = 0$$

**Capacitor**

$$P = \frac{V_m I_m}{2} \cos 90^\circ = 0$$

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and Phasor Concept

11

## 1.2.3 Rectangular and Polar Representation


$$\dot{C} = A + jB \quad \text{Rectangular form}$$

$$\dot{C} = C \angle \theta \quad \text{Polar form}$$

**Polar to rectangular**

$$A = C \cos \theta$$

$$B = C \sin \theta$$

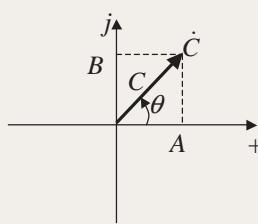

**Rectangular to polar**

$$C = \sqrt{A^2 + B^2}, \theta = \tan^{-1} \frac{B}{A}$$

Example:

$$v_1 = V_{m1} \sin(\omega t + \theta_1) \sum V_{m1} \angle \theta_1$$

$$v_2 = V_{m2} \sin(\omega t + \theta_{21}) \sum V_{m2} \angle \theta_2$$

$$v = v_1 + v_2 = V_{m1} \angle \theta_1 + V_{m2} \angle \theta_2$$

Use the calculator directly with polar form or convert  $v_1$  and  $v_2$  to rectangular form, do the summation and convert the result to polar form.

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and Phasor Concept

12

## 1.2.4 Impedance and Phasor Diagram

**Resistor:**  $\dot{V} = I\dot{Z}_R \sum \dot{Z}_R = R\langle 0^\circ = R + j0$   
 $I_m = \frac{V_m}{R}$  or  $V_m = I_m R$       In phasor form  $\dot{V} = V\langle 0^\circ \sum \dot{I} = \frac{V}{R}\langle 0^\circ = I\langle 0^\circ$

**Inductor:**  $\dot{V} = I\dot{Z}_L \sum \dot{Z}_L = X_L\langle +90^\circ = \omega L\langle +90^\circ = 0 + jX_L$   
 $I_m = \frac{V_m}{\omega L}$  or  $V_m = I_m X_L$   
In phasor form  $\dot{V} = V\langle 0^\circ \sum \dot{I} = \frac{V}{X_L}\langle -90^\circ = I\langle -90^\circ$

**Capacitor:**  $\dot{V} = I\dot{Z}_C \sum \dot{Z}_C = X_C\langle -90^\circ = \frac{1}{\omega C}\langle -90^\circ = 0 - jX_C$   
 $I_m = \omega C V_m$  or  $V_m = I_m X_C$   
In phasor form  $\dot{V} = V\langle 0^\circ \sum \dot{I} = \frac{V}{X_C}\langle +90^\circ = I\langle +90^\circ$

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

13

## 1.2.5 Kirchhoff's Laws

- **Voltage Law:** the complex (vector) sum of the potential rises and drops around a closed loop (or path) is zero.

$$\sum_o V = 0 \Leftrightarrow \sum_o V_{rise} = \sum_o V_{drops}$$

- **Current Law:** the complex (vector) sum of the currents entering and leaving a junction is zero. Or the sum of currents entering a junction must equal the sum of currents leaving the junction.

$$\sum I_{entering} = \sum I_{leaving}$$

Dr. Adel Gastli


Sinusoidal Alternating Waveforms and  
Phasor Concept

14

# 1.3 Series and Parallel Circuits
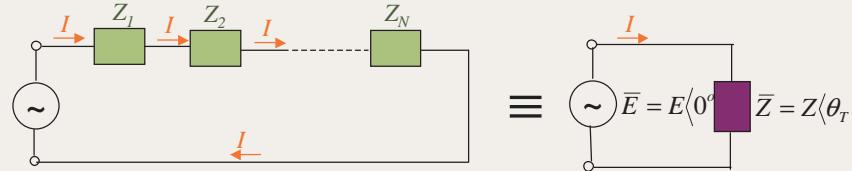
## 1.3.1 Series Circuits

*Two elements are in series if they have only one point of intersection that is not connected to other current-carrying elements of the network.*



For  $N$  impedances in series the equivalent impedance is:

$$\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 + \dots + \bar{Z}_N = Z_T \angle \theta_T$$

Impedance amplitude
Impedance angle

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

15

Current in the circuit:  $\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{E \angle 0^\circ}{Z_T \angle \theta_T} = I \angle -\theta_T$  (A)

Voltage across each element:  $\bar{V}_1 = \bar{I} \bar{Z}_1, \bar{V}_2 = \bar{I} \bar{Z}_2, \dots, \bar{V}_N = \bar{I} \bar{Z}_N$  (V)

Power delivered by each impedance :  $P_i = I^2 R_i$  (W) ( $i = 1, \dots, N$ )


Power delivered by the source:  $P_T = EI \cos \theta_T = P_1 + P_2 + \dots + P_N$  (W)

Dr. Adel Gastli


Sinusoidal Alternating Waveforms and  
Phasor Concept

16

### Example of Series R-L Circuit:

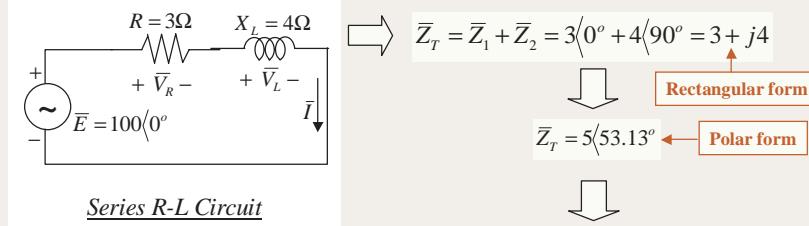

Impedance diagram:

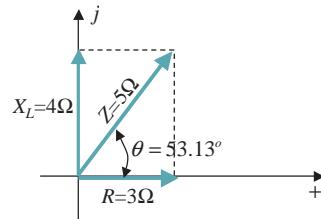

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

17

Current:  $\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{100\langle 0^\circ \rangle}{5\langle 53.13^\circ \rangle} = 20\langle -53.13^\circ \rangle \text{ (A)}$

#### Voltages:

Polar form:

$$\bar{V}_R = \bar{I}\bar{Z}_1 = 20\langle -53.13^\circ \times 3\langle 0^\circ \rangle = 60\langle -53.13^\circ \rangle \text{ (V)}$$

$$\bar{V}_L = \bar{I}\bar{Z}_2 = 20\langle -53.13^\circ \times 4\langle 90^\circ \rangle = 80\langle +36.87^\circ \rangle \text{ (V)}$$


Rectangular form:

$$\bar{V}_R = 36 - j48 \text{ (V)}$$

$$\bar{V}_L = 64 + j48 \text{ (V)}$$

Apply Kirchhoff's voltage law:  $\sum_{\text{o}} \bar{V} = \bar{E} - \bar{V}_R - \bar{V}_L = 0 \Rightarrow \bar{E} = \bar{V}_R + \bar{V}_L$   
 $\bar{E} = (36 - j48) + (64 + j48) = 100 + j0 = 100\langle 0^\circ \rangle$

#### Phasor diagram:

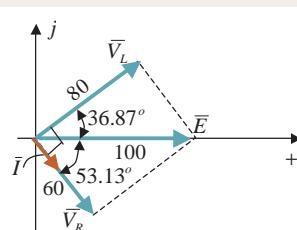

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

18

**Power:**

Method 1:  $P_T = EI \cos \theta_T = 100 \times 20 \times \cos(53.13^\circ) = 1200 \text{ W}$

Method 2:  $P_T = I^2 R = 20^2 \times 3 = 1200 \text{ W}$


Method 3:  $P_T = EI \cos \theta_T = P_R + P_L = V_R I \cos \theta_R + V_L I \cos \theta_L$   
 $= 60 \times 20 \times \cos 0^\circ + 80 \times 20 \times \cos 90^\circ$   
 $= 1200 + 0 = 1200 \text{ W}$

**Power Factor:**  $PF = \frac{P_T}{EI} = \cos \theta = \cos -53.13^\circ = 0.6 \text{ lagging}$

↑  
Impedance angle = angle between input voltage and current

When current is lagging the voltage, the power factor is said to be a:  
*lagging power factor.*

### Example of Series R-L-C Circuit:

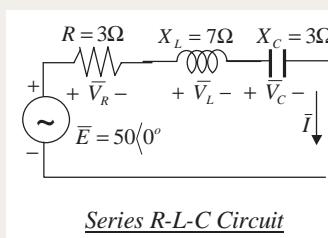


$$\begin{aligned} \bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3 = R\langle 0^\circ \rangle + X_L\langle 90^\circ \rangle + X_C\langle -90^\circ \rangle \\ &= 3 + j7 - j3 = 3 + j4 \end{aligned}$$

Rectangular form

$\bar{Z}_T = 5\langle 53.13^\circ \rangle$  Polar form

Impedance diagram:

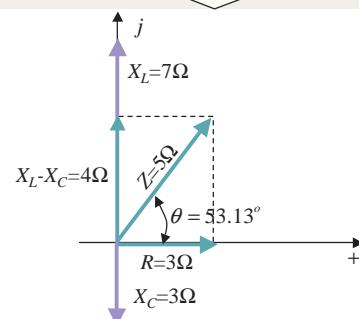

**Current:**  $\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{50\langle 0^\circ \rangle}{5\langle 53.13^\circ \rangle} = 10\langle -53.13^\circ \rangle \text{ (A)}$

**Voltages:**

Polar form:

$$\bar{V}_R = \bar{I}\bar{Z}_1 = 10\langle -53.13^\circ \times 3\langle 0^\circ \rangle = 30\langle -53.13^\circ \rangle \text{ (V)}$$

$$\bar{V}_L = \bar{I}\bar{Z}_2 = 10\langle -53.13^\circ \times 7\langle 90^\circ \rangle = 70\langle +36.87^\circ \rangle \text{ (V)}$$

$$\bar{V}_C = \bar{I}\bar{Z}_3 = 10\langle -53.13^\circ \times 3\langle -90^\circ \rangle = 30\langle -143.13^\circ \rangle \text{ (V)}$$

Rectangular form:

$$\bar{V}_R = 18 - j24 \text{ (V)}$$

$$\bar{V}_L = 56 + j42 \text{ (V)}$$


$$\bar{V}_C = -24 - j18 \text{ (V)}$$

Apply Kirchhoff's voltage law:

$$\sum_o \bar{V} = \bar{E} - \bar{V}_R - \bar{V}_L - \bar{V}_C = 0 \quad \sum \bar{E} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

$$\bar{E} = (18 - j24) + (56 + j42) + (-24 - j18) = 50 + j0 = 50\langle 0^\circ \rangle$$

**Phasor diagram:**

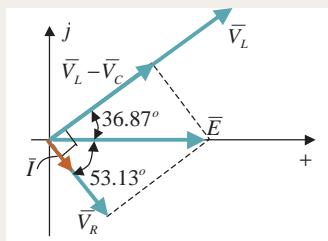


**Time domain:**

$$i = \sqrt{2} \times 10 \sin(\omega t - 53.13^\circ)$$

$$v_R = \sqrt{2} \times 30 \sin(\omega t - 53.13^\circ)$$

$$v_L = \sqrt{2} \times 70 \sin(\omega t + 36.87^\circ)$$
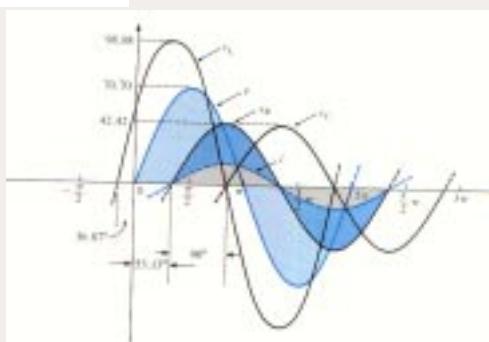
$$v_C = \sqrt{2} \times 30 \sin(\omega t - 143.13^\circ)$$



### Power:

$$\text{Method 1: } P_T = EI \cos \theta_T = 50 \times 10 \times \cos(53.13^\circ) = 300 \text{ W}$$

$$\text{Method 2: } P_T = I^2 R = 10^2 \times 3 = 300 \text{ W}$$

$$\begin{aligned} \text{Method 3: } P_T &= EI \cos \theta_T = P_R + P_L + P_C = V_R I \cos \theta_R + V_L I \cos \theta_L + V_C I \cos \theta_C \\ &= 30 \times 10 \times \cos 0^\circ + 70 \times 10 \times \cos 90^\circ + 30 \times 10 \times \cos 90^\circ \\ &= 300 + 0 + 0 = 300 \text{ W} \end{aligned}$$

### Power Factor:

$$PF = \frac{P_T}{EI} = \cos \theta = \frac{R}{Z_T}$$


↑  
Impedance angle = angle between input voltage and current

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept


23

### Voltage Divider Rule:

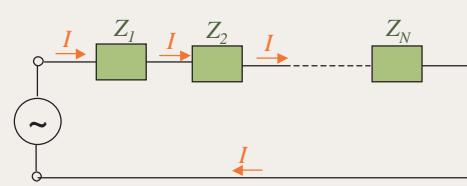

$$\begin{aligned} I &= \frac{E}{Z_T} = \frac{V_i}{Z_i} \\ V_i &= \frac{Z_i E}{Z_T} \end{aligned}$$

### Example:

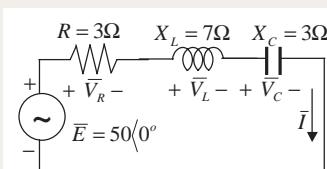

$$\begin{aligned} V_R &= \frac{Z_R E}{Z_T} = \frac{RE}{R + jX_L - jX_C} = \frac{3 \times 50}{3 + j(7-3)} = \frac{150}{5\sqrt{53.13^\circ}} = 30\angle -53.13^\circ \\ V_L &= \frac{Z_L E}{Z_T} = \frac{jX_L E}{R + jX_L - jX_C} = \frac{7\angle 90^\circ \times 50}{3 + j(7-3)} = \frac{350\angle 90^\circ}{5\sqrt{53.13^\circ}} = 70\angle 36.87^\circ \\ V_C &= \frac{Z_C E}{Z_T} = \frac{-jX_C E}{R + jX_L - jX_C} = \frac{3\angle -90^\circ \times 50}{3 + j(7-3)} = \frac{150\angle 90^\circ}{5\sqrt{53.13^\circ}} = 30\angle -143.13^\circ \end{aligned}$$

Series R-L-C Circuit


Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept


24
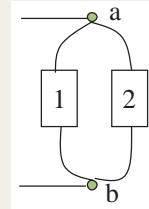
## 1.3.2 Parallel Circuits

*Two elements, branches, or networks are in parallel if they have two points in common.*



Parallel Impedances:

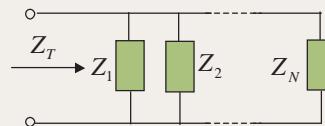

$$Y_i = \frac{1}{Z_i} = \text{Admittance}$$

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \quad \Rightarrow \quad Y_T = Y_1 + Y_2 + \dots + Y_N$$

Total impedance of parallel impedances is always less than the value of the smallest impedance

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and Phasor Concept

25


For two parallel impedances:  $Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$

For three parallel impedances:  $Z_T = \frac{Z_1 Z_2 Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}$

Conductance:  $G = \frac{1}{R}$  (siemens, S)

Susceptance:  $B_L = \frac{1}{X_L}$  (siemens, S)

$B_C = \frac{1}{X_C}$  (siemens, S)

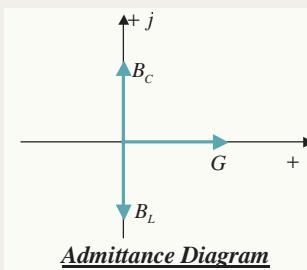


Dr. Adel Gastli


Sinusoidal Alternating Waveforms and Phasor Concept

26

### Example of Parallel R-L-C Circuit:

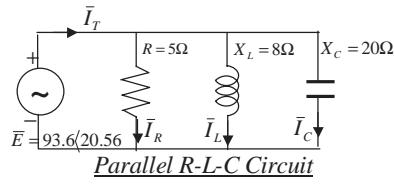
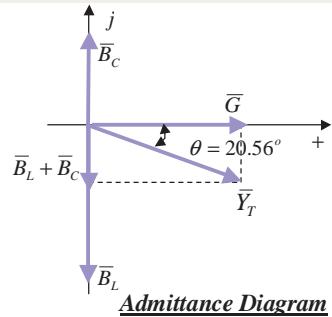
$$\begin{aligned}\bar{Y}_1 &= \bar{G} = G\langle 0^\circ = \frac{1}{R} \langle 0^\circ = 0.2 \langle 0^\circ \\ \bar{Y}_2 &= \bar{B}_L = B_L \langle -90^\circ = \frac{1}{X_L} \langle -90^\circ = 0.125 \langle -90^\circ \\ \bar{Y}_3 &= \bar{B}_C = B_C \langle 90^\circ = \frac{1}{X_C} \langle 90^\circ = 0.05 \langle 90^\circ\end{aligned}$$



$$\begin{aligned}\bar{Y}_T &= \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 = (0.2 + j0) + (0 - j0.125) + (0 + j0.05) \\ &= 0.2 - j0.075 = 0.2136 \langle -20.56^\circ\end{aligned}$$

$$\bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.2136 \langle -20.56^\circ} = 4.68 \langle 20.56^\circ$$

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

27

### Current:

$$\bar{I}_T = \frac{\bar{E}}{\bar{Z}_T} = \frac{93.6 \langle 20.56^\circ}{4.68 \langle 20.56^\circ} = 20 \langle 0^\circ$$

$$\bar{I}_R = \bar{E} \bar{G} = 93.6 \langle 20.56^\circ \times 0.2 \langle 0^\circ = 18.72 \langle 20.56^\circ$$

$$\bar{I}_L = \bar{E} \bar{B}_L = 93.6 \langle 20.56^\circ \times 0.125 \langle -90^\circ = 11.7 \langle 69.44^\circ$$

$$\bar{I}_C = \bar{E} \bar{B}_C = 93.6 \langle 20.56^\circ \times 0.05 \langle 90^\circ = 4.68 \langle 110.56^\circ$$

Apply Kirchhoff's current law:


$$\begin{aligned}\bar{I}_T &= \bar{I}_R + \bar{I}_L + \bar{I}_C \quad \bar{I}_T - \bar{I}_R - \bar{I}_L - \bar{I}_C = 0 \\ (20 + j0) &- (17.527 + j6.574) - (4.109 - 10.955) - (-1.643 + j4.382) \equiv 0 + j0\end{aligned}$$

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

28


## Current Divider Rule:

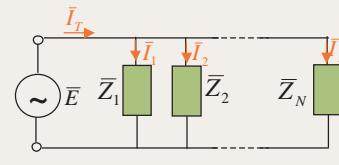

$$\bar{E} = \bar{I}_T Z_T = \bar{I}_i \bar{Z}_i$$

$$\bar{I}_i = \frac{\bar{Z}_T \bar{I}_T}{\bar{Z}_i}$$

### Example:

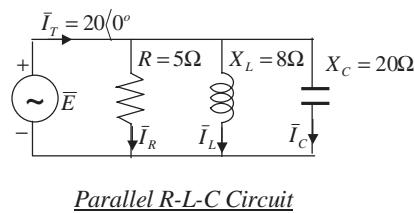

$$\bar{Z}_T = 4.68 \angle 20.56^\circ$$

$$\bar{I}_R = \frac{\bar{Z}_T \bar{I}_T}{\bar{Z}_R} = \frac{4.68 \angle 20.56^\circ \times 20 \angle 0^\circ}{5 \angle 0^\circ} = 18.72 \angle 20.56^\circ$$

$$\bar{I}_L = \frac{\bar{Z}_T \bar{I}_T}{\bar{Z}_L} = \frac{4.68 \angle 20.56^\circ \times 20 \angle 0^\circ}{8 \angle 90^\circ} = 11.7 \angle -69.44^\circ$$

$$\bar{I}_C = \frac{\bar{Z}_T \bar{I}_T}{\bar{Z}_C} = \frac{4.68 \angle 20.56^\circ \times 20 \angle 0^\circ}{20 \angle -90^\circ} = 4.68 \angle 110.56^\circ$$

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

29

## Summary:

**Kirchhoff's law applies to ac circuits the same way it applies to dc circuits.**

**Series and parallel circuit rules apply to ac circuits the same way they apply to dc circuits. Instead of resistance R impedance Z is used.**

$$\begin{array}{l} \text{Series} \\ Z_T = \sum_{i=1}^N Z_i \end{array} \quad \text{impedance}$$

$$\begin{array}{l} \text{Parallel} \\ \bar{Y}_T = \frac{1}{\bar{Z}_T} = \sum_{i=1}^N \frac{1}{\bar{Z}_i} \end{array} \quad \text{admittance}$$

**For any network configuration(series, parallel or series-parallel), the angle  $\theta_T$  by which the applied voltage leads the source current will be positive for inductive network and negative for capacitive networks.**

Dr. Adel Gastli

Sinusoidal Alternating Waveforms and  
Phasor Concept

30