

## AVERAGE POWER

The instantaneous power to the load is  $P = v i$

In general:  $v = V_m \sin(\omega t + \theta)$  and  $i = I_m \sin(\omega t)$


Therefore,

$$p = \left[ \frac{V_m I_m}{2} \cos(\theta) \right] - \frac{V_m I_m}{2} \cos(\theta) \cos(2\omega t) + \frac{V_m I_m}{2} \sin(\theta) \sin(2\omega t)$$

The first term in the preceding equation has a constant magnitude (no time dependence) and therefore provides some net transfer of energy.

This term is referred to as the *average Power or real Power*.

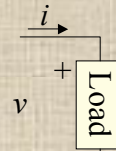since  $V_{eff} = \frac{V_m}{\sqrt{2}}$  and  $I_{eff} = \frac{I_m}{\sqrt{2}}$   $\longrightarrow$   $P = V_{eff} I_{eff} \cos \theta$




## Resistor

$V$  and  $I$  are in phase  $\longrightarrow \theta = 0$

$$\therefore P = V_{eff} I_{eff} = \frac{V_{eff}^2}{R} = I_{eff}^2 R = I^2 R$$

The energy dissipated by the resistor over one full cycle of the power curve:

$$P = V_{eff} I_{eff} T_2 = V I T_2$$

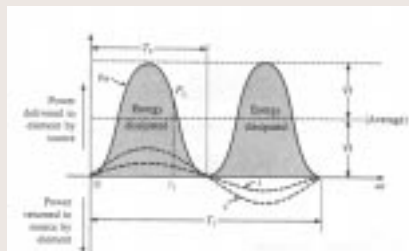

### Inductor

$I$  lags  $V$  by  $90^\circ$   $\longrightarrow \theta = 90$

$$\therefore P = V_{eff} I_{eff} \cos(90) = 0$$

### Capacitor

$I$  leads  $V$  by  $90^\circ$   $\longrightarrow \theta = 90$

$$\therefore P = V_{eff} I_{eff} \cos(90) = 0$$

### POWER FACTOR

$$\text{Power factor} = F_p = \cos \theta = \frac{P}{VI}$$

The power factor can be leading or lagging.

- The more reactive a load, the lower the power factor, and the smaller the average power delivered.
- Low power factor are usually avoided, since a high current would be required to deliver any appreciable power. This higher current demand produces higher heating losses and, consequently, the system operates at a lower efficiency.
- Capacitive networks have leading power factors, and inductive networks have lagging power factors.

### APPARENT POWER

It is the product of voltage and current, its units are *volts-amperes*. Its magnitude is determined by:

$$S = VI$$

The average power is defined by:

$$P = VI \cos \theta$$

Therefore,

$$P = S \cos \theta$$

Or the power factor of a system is

$$F_p = \cos \theta = \frac{P}{S}$$

### REACTIVE POWER

The reactive power is defined as:

$$Q = VI \sin(\theta)$$

For Inductor,  $\theta = 90$

$$Q_L = VI = I^2 X_L = \frac{V^2}{X_L}$$

$$W_L = LI^2$$

For Capacitor,  $\theta = 90$

$$Q_c = VI = I^2 X_c = \frac{V^2}{X_c}$$

$$W_L = CV^2$$


### THE POWER TRIANGLE

The average power, apparent power and reactive power can be related by

$$S = P + JQ$$


For an inductive load

$$S = P + JQ_L$$

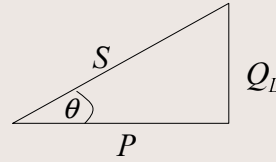


For a capacitive load

$$S = P - JQ_c$$

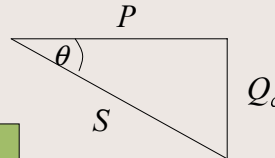


The three powers are related by the Pythagorean theorem;

$$S^2 = P^2 + Q^2$$

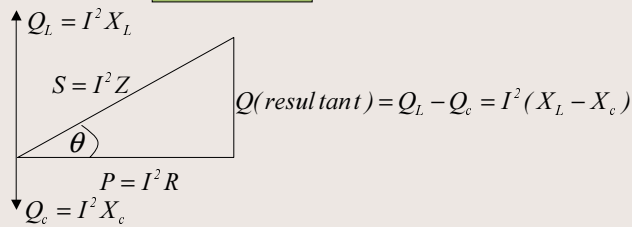

### POWER FACTOR CORRECTION

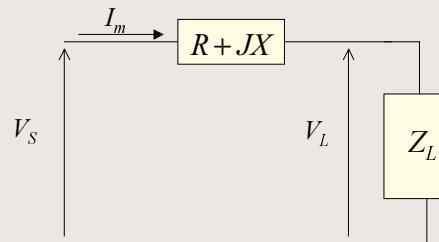

$V_L$  is constant

Power absorbed by the line (P losses) =  $I_m^2 R$

Power delivered to the load =  $P_L = V_L I_m \cos(\theta)$

$$I_m = \frac{P_L}{V_L \cos(\theta)} \quad \longrightarrow \quad \cos(\theta) \uparrow \Rightarrow I_m \downarrow \Rightarrow P \text{ Losses } \downarrow$$

How could we improve the power factor? Usually by connecting a capacitor in parallel with the loads.

The process of introducing reactive elements to bring the power factor closer to unity is called power-factor correction.