

**Sultan Qaboos University**  
**College of Engineering**  
**Electrical and Electronics Engineering Department**

**Quiz #1 With Typical Answers**

<b>Course Code</b> : Electric Circuits II	<b>Instructor</b> : Dr. Adel Gastli
<b>Course Code</b> : ELEC3122	<b>Date</b> : Tue. 27-06-2000
<b>Semester</b> : Summer 2000	<b>Time</b> : 20 min

**Student name:**

**Marks**

**Student ID No.:**

/
100

**Questions**

For the circuit in Fig. 1:

1. Find the total admittance  $\bar{Y}_T$  in polar form.
2. Sketch the admittance diagram.
3. Find the value of  $C$  in microfarads and  $L$  in henries.
4. Find the current  $i_T$  and current  $i_R$ ,  $i_L$ , and  $i_C$  in Phasor form.
5. Sketch the Phasor diagram of the currents  $\bar{I}_T$ ,  $\bar{I}_R$ ,  $\bar{I}_L$ , and  $\bar{I}_C$  and the voltage  $\bar{E}$ .

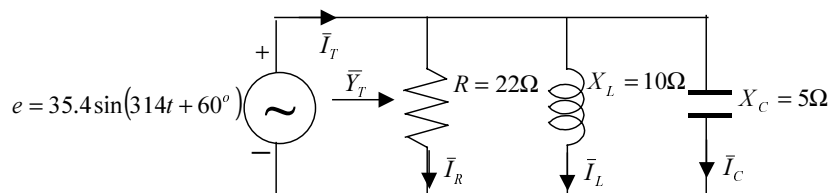


Fig. 1

**Answers**

1. The equivalent total admittance is calculated as follows:


$$\bar{Y}_1 = \frac{1}{R} = \frac{1}{22} = 0.04545 \angle 0^\circ = 0.0454 + j0$$

$$\bar{Y}_2 = \frac{1}{jX_L} = \frac{1}{10 \angle 90^\circ} = 0.1 \angle -90^\circ = 0 - j0.1$$

$$\bar{Y}_3 = \frac{1}{-jX_C} = \frac{1}{5 \angle -90^\circ} = 0.2 \angle 90^\circ = 0 + j0.2$$

$$\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 = 0.04545 + j0.1 = 0.11 \angle 65.56^\circ$$

2. The admittance diagram is as follows:

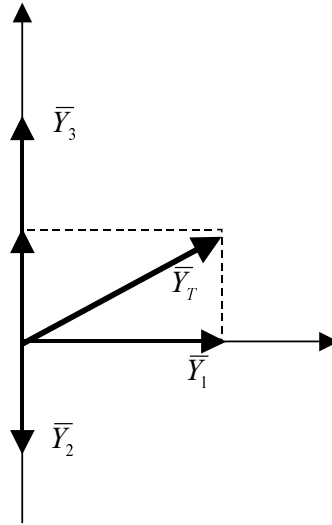

3. The capacitor and inductance values are determined as follows:

$$\omega = 314$$

$$X_L = \omega L = 10 \Rightarrow L = \frac{X_L}{\omega} = \frac{10}{314} = 0.032\text{H}$$

$$X_C = \frac{1}{\omega C} = 5 \Rightarrow C = \frac{1}{314 \times 5} = 0.637 \times 10^{-3} \text{ F} = 637 \mu\text{F}$$

4. The branches currents are calculated as follows:

$$\bar{E} = \frac{35.4}{\sqrt{2}} [60^\circ] = 25 [60^\circ]$$

$$\bar{I}_T = \bar{E} \times \bar{Y}_T = 25 [60^\circ] \times 0.11 [65.56^\circ] = 2.75 [125.56^\circ]$$

$$\bar{I}_R = \bar{E} \times \bar{Y}_R = 25 [60^\circ] \times 0.04545 [0^\circ] = 1.14 [60^\circ]$$

$$\bar{I}_L = \bar{E} \times \bar{Y}_L = 25 [60^\circ] \times 0.1 [-90^\circ] = 2.5 [-30^\circ]$$

$$\bar{I}_C = \bar{E} \times \bar{Y}_C = 25 [60^\circ] \times 0.2 [90^\circ] = 5 [150^\circ]$$

5. The phasor diagram is sketched as follows:

